

# Arithmetic Logic Unit (ALU)

---

Dr. Igor Ivkovic

iivkovic@uwaterloo.ca

[with material from “Computer Organization and Design” by Patterson and Hennessy, and “Digital Design and Computer Architecture” by Harris and Harris, both published by Morgan Kaufmann]

# Objectives

---

- Binary Representations of Integers
- Basic Arithmetic Circuitry
- Composing Arithmetic Logic Unit (ALU)
- Multipliers and Dividers

# Unsigned Binary Integers

---

## ■ Given an n-bit number:

$$x = x_{n-1}2^{n-1} + x_{n-2}2^{n-2} + \dots + x_12^1 + x_02^0$$

- No sign bit present
- Range: 0 to  $+2^n - 1$

## ■ Example:

- 0000 0000 0000 0000 0000 0000 0000 1011<sub>2</sub>  
= 0 + ... + 1×2<sup>3</sup> + 0×2<sup>2</sup> + 1×2<sup>1</sup> + 1×2<sup>0</sup>  
= 0 + ... + 8 + 0 + 2 + 1 = 11<sub>10</sub>

## ■ Using 32 bits:

- Represent 0 to +4,294,967,295
- How do we represent negative numbers?

# One Idea: Signed/Magnitude Binary Integers

---

## ■ Given an n-bit number:

$$X = x_{n-1}2^{n-1} + x_{n-2}2^{n-2} + \dots + x_12^1 + x_02^0$$

- Left-most bit represents the sign (1 for negative, 0 for non-negative)
- Range:  $-2^{n-1} + 1$  to  $+2^{n-1} - 1$  (cannot represent  $-2^{n-1}$  and  $2^{n-1}$ )

## ■ Example:

- $\underline{1}000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1011_2$   
 $= -(0 + \dots + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0)$   
 $= -(0 + \dots + 8 + 0 + 2 + 1) = -11_{10}$

## ■ Using 32 bits with signed/magnitude representation:

- Represent  $-2,147,483,647$  to  $+2,147,483,647$
- 0 is represented twice as  $1000\dots0000_2$  and  $0000\dots0000_2$
- Not trivial to perform arithmetic operations such as addition and subtraction

# Better Idea: Two's Complement Integers /1

## ■ Given an n-bit number:

$$X = x_{n-1}2^{n-1} + x_{n-2}2^{n-2} + \dots + x_12^1 + x_02^0$$

- Left-most bit represents the sign (1 for negative, 0 for non-negative)
- Range:  $-2^{n-1}$  to  $+2^{n-1} - 1$  (**cannot represent  $2^{n-1}$** )

## ■ Example:

$$\begin{aligned} & \underline{1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1100}_2 \\ & \equiv -1 \times 2^{31} + 1 \times 2^{30} + \dots + 1 \times 2^2 + 0 \times 2^1 + 0 \times 2^0 \\ & = -2,147,483,648 + 2,147,483,644 = -4_{10} \end{aligned}$$

Multiply  
by -1

## ■ Using 32 bits

- Represent  $-2,147,483,648$  to  $+2,147,483,647$
- 0 is represented only once as  $0000\dots0000_2$
- Easier to perform arithmetic operations such as addition and subtraction (see the discussion that follows)

# Better Idea: Two's Complement Integers /2

---

## ■ Bit 31 or the left-most bit:

- The most significant bit (MSB) or the sign bit

MSB

1111 1111 1111 1111 1111 1111 1100<sub>2</sub>

- MSB = 1 for negative numbers
- MSB = 0 for non-negative numbers

## ■ Non-negative numbers have the same unsigned and two's complement representation

## ■ Compute the negative value when MSB = 1:

- Start with  $-2^{n-1}$  and add  $+2^k$  for each k-th bit from  $n-2$  to 0 that is 1; ignore the bits that are not 1

## ■ Example:

- Start with  $1100_2 = -2^3 + 2^2 = -8 + 4 = -4_{10}$

# Better Idea: Two's Complement Integers /3

---

## ■ Some specific numbers:

- Most positive: 0111 1111 ... 1111
- 2: 0000 0000 ... 0010
- 1: 0000 0000 ... 0001
- 0: 0000 0000 ... 0000
- -1: 1111 1111 ... 1111
- -2: 1111 1111 ... 1110
- -3: 1111 1111 ... 1101
- -4: 1111 1111 ... 1100
- -5: 1111 1111 ... 1011
- -6: 1111 1111 ... 1010
- -7: 1111 1111 ... 1001
- -8: 1111 1111 ... 1000
- Most negative: 1000 0000 ... 0000

**Notice the pattern for the negative numbers: counting the binary numbers in reverse**

# Signed Negation

---

## ■ How to negate a signed integer?

- **Easy: Compute the complement and add 1**
- Compute the complement means convert  $1 \rightarrow 0$  and  $0 \rightarrow 1$

$$x + \bar{x} = 1111\dots111_2 = -1$$

$$\bar{x} + 1 = -x$$

## ■ Example: Negate +2

- $+2 = 0000\ 0000 \dots 0010_2$
- $-2 = 1111\ 1111 \dots 1101_2 + 1$   
 $= 1111\ 1111 \dots 1110_2$
- Interesting: What if you have to negate 0?



# Sign Extension

---

- **Representing a number using more bits**
  - The first goal is to preserve the numeric value
- **How to extend the bit representation?**
  - Fill the extra bit slots with the MSB (the sign bit)
  - For the unsigned values, fill the extra slots with 0
- **Example: 4-bit to 8-bit**
  - +5: 0101 => 0000 0101
  - -5: 1011 => 1111 1011
- **Example: 8-bit to 16-bit**
  - +2: 0000 0010 => 0000 0000 0000 0010
  - -2: 1111 1110 => 1111 1111 1111 1110

# Logical Operations

---

## ■ Instructions for bitwise manipulation:

Operation	C	Java	MIPS
Shift left	<<	<<	sll
Shift right	>>	>>>	srl
Bitwise AND	&	&	and, andi
Bitwise OR			or, ori
Bitwise NOT	~	~	nor

- Useful for extracting and inserting groups of bits in a word
- **MIPS instructions discussed later in the course**

# Shift Operations

---

## ■ Shift left logical (sll)

- Shift left and fill with 0 bits
- sll by  $i$  bits multiplies by  $2^i$
- Example:  $11001 \ll 2 = 00100$

## ■ Shift right logical (srl)

- Shift right and fill with 0 bits
- srl by  $i$  bits divides by  $2^i$  (unsigned only)
- Example:  $11001 \gg 2 = 00110$

## ■ We will use shifters in creation of multipliers

- More on shifters in the context of MIPS later in the course

# AND Operation

---

## ■ AND Operation

- Useful to mask bits in a word
- Select some bits, clear others to 0
- MIPS: `and $t0, $t1, $t2`

\$t2	0000	0000	0000	0000	0000	1101	1100	0000
\$t1	0000	0000	0000	0000	0011	1100	0000	0000
\$t0	0000	0000	0000	0000	0000	1100	0000	0000

# OR Operation

---

## ■ OR Operation

- Useful to include bits in a word
- Set some bits to 1, leave others unchanged
- MIPS: `or $t0, $t1, $t2`

\$t2	0000	0000	0000	0000	0000	1101	1100	0000
\$t1	0000	0000	0000	0000	0011	1100	0000	0000
\$t0	0000	0000	0000	0000	0011	1101	1100	0000

# NOT Operation

## ■ NOT Operation

- Useful to invert bits in a word
- Change 0 to 1, and 1 to 0
- MIPS has a NOR 3-operand instruction
- $a \text{ NOR } b == \text{NOT} (a \text{ OR } b)$
- MIPS : `nor $t0, $t1, $0`

Register \$0 always  
reads zero

\$t1	0000	0000	0000	0000	0011	1100	0000	0000
\$t0	1111	1111	1111	1111	1100	0011	1111	1111

# Arithmetic Circuitry

---

- **Digital building blocks:**

- So far, we have covered gates, multiplexers, decoders, and registers
- We will use these to build arithmetic circuits, counters, memory arrays, and logic arrays

- **Digital building blocks demonstrate hierarchy, modularity, and regularity:**

- Hierarchy of simpler components
- Well-defined interfaces and functions
- Regular structure easily extends to different sizes


- **We will use all of these building blocks to create a microprocessor**

# Adders /1

## ■ Adders:

- Add two input bits, A and B, and output the result, S
- If there is carry-over, it is outputted as  $C_{out}$
- Carry-over is added to the next adder in the chain, or it indicates overflow if it is the last adder in the chain

### Half Adder

 


A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

S =  
 $C_{out}$  =

Carry-over when A and B are both 1

### Full Adder

 

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S =  
 $C_{out}$  =



# Adders /2


## ■ Adders:

- Half adder has no carry-over input from the previous adder
- Full adder represents a chained adder and input from the previous adder is given as  $C_{in}$

## ■ How to create an adder from gates?

- Use the logical formulas shown below each truth table

### Half Adder

 


A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

### Full Adder

 

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

# Adders /3


---

## ■ Multibit Adders (CPAs)

- When composing multibit adders, different strategies for propagating carry-over bits apply
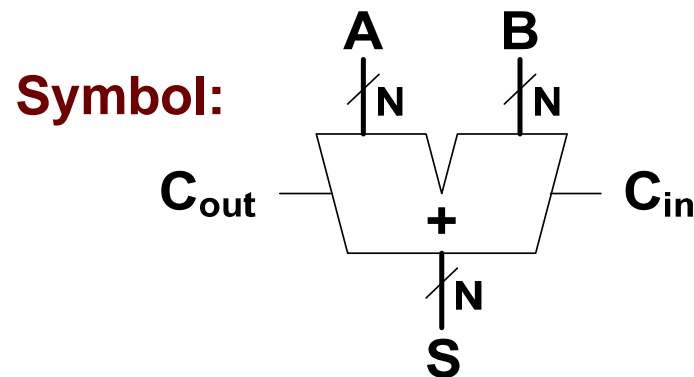
## ■ Types of carry propagate adders (CPAs):


- Ripple-carry (slow)
- Carry-lookahead (fast)
- Prefix (faster)
- Carry-lookahead and prefix adders can perform faster for large adders but require more hardware



# Ripple-Carry Adder
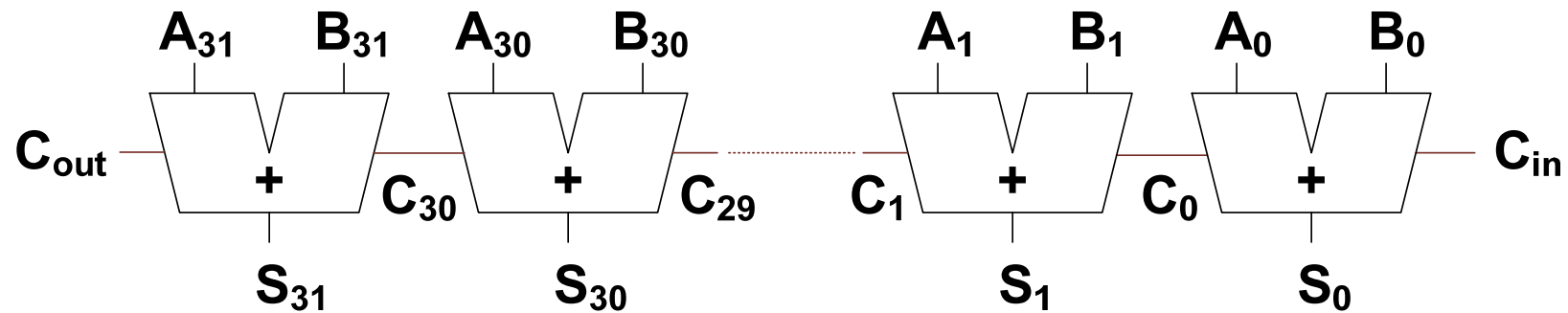
## ■ Ripple-Carry Adder

- Simply chain 1-bit adders together
- Carry ripples through entire chain
- Advantage: simpler operational semantics
- Disadvantage: slower performance



## ■ Ripple-Carry Adder Delay

- $t_{\text{ripple}} = N \times t_{FA}$ , where  $t_{FA}$  is the delay of a full adder

# Carry-Lookahead Adder /1

---



## ■ Carry-Lookahead Adder

- Instead of waiting for each adder to compute the carry-out bit, divide the addition into k-bit blocks and precompute carry-outs
- Compute carry-out ( $C_{out}$ ) for k-bit blocks using generate,  $G_i$ , and propagate,  $P_i$ , signals

## ■ Operational Semantics:

- Column i adder produces a carry-out by either generating a carry-out or propagating a carry-in to the carry-out
- Generate ( $G_i$ ) and propagate ( $P_i$ ) signals for each column:
  - Column i will generate a carry-out if  $A_i$  AND  $B_i$  are both 1  
 $G_i = A_i B_i$
  - Column i will propagate a carry-in to the carry-out if  $A_i$  OR  $B_i$  is 1  
 $P_i = A_i + B_i$
  - The carry-out of column i ( $C_i$ ) is:  
 $C_i = A_i B_i + (A_i + B_i)C_{i-1} = G_i + P_i C_{i-1}$

# Carry-Lookahead Adder /2

 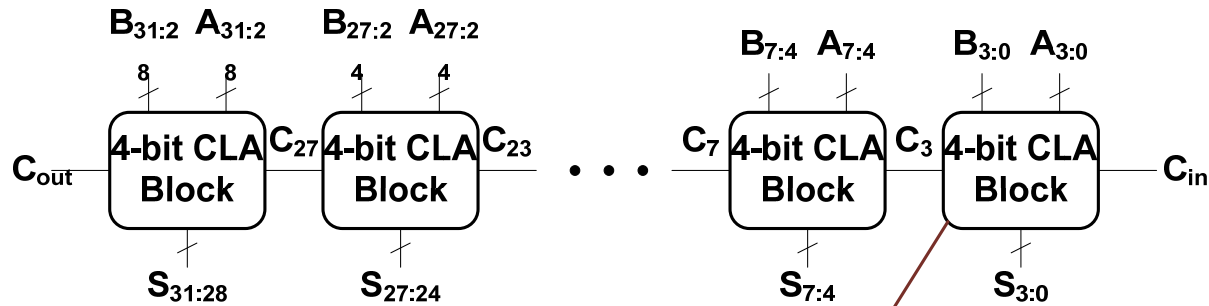

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$

$$C_i = A_i B_i + (A_i + B_i)C_{i-1} \\ = G_i + P_i C_{i-1}$$

**Example (in class):**

**A = 0001**

**B = 1111**

**C<sub>out</sub> = 1**

# Carry-Lookahead Adder /3

---

## ■ Operational Semantics Continued:

- Step 1. Compute  $G_i$  and  $P_i$  for all columns
- Step 2. Compute  $G$  and  $P$  for  $k$ -bit blocks
- Step 3.  $C_{in}$  propagates through each  $k$ -bit  $P/G$  block

## ■ Example: 4-bit blocks ( $G_{3:0}$ and $P_{3:0}$ )

- $G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$
- $P_{3:0} = P_3 P_2 P_1 P_0$

## ■ Generally, as shown on the previous slide:

- $G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} G_j))$
- $P_{i:j} = P_i P_{i-1} P_{i-2} P_j$
- $C_i = G_{i:j} + P_{i:j} C_{i-1}$

# Carry-Lookahead Adder /4

---

## ■ Carry-Lookahead Adder Delay

- For N-bit CLA with k-bit blocks:

$$t_{\text{CLA}} = t_{\text{pg}} + t_{\text{pg\_block}} + (N/k - 1) \times t_{\text{AND\_OR}} + k \times t_{\text{FA}}$$

- where  $t_{\text{pg}}$  is the delay needed to generate all  $P_i, G_i$
- $t_{\text{pg\_block}}$  is the delay needed to generate all  $P_{i:j}, G_{i:j}$
- $t_{\text{AND\_OR}}$  is the delay from  $C_{\text{in}}$  to  $C_{\text{out}}$  of final AND/OR gate in k-bit CLA block

- An N-bit CLA is generally much faster than a ripple-carry adder for  $N > 16$

# Prefix Adder /1

---



## ■ Prefix Adder

- Continues on the idea of carry-lookahead adder
- Computes carry-in ( $C_{i-1}$ ) for each column then computes the sum  $S_i = (A_i \oplus B_i) \oplus C_i$
- Computes G and P for 1-, 2-, 4-, 8-, etc bit blocks until all  $G_i$  (carry-in) are known (**computed in  $\log_2 N$  stages**)
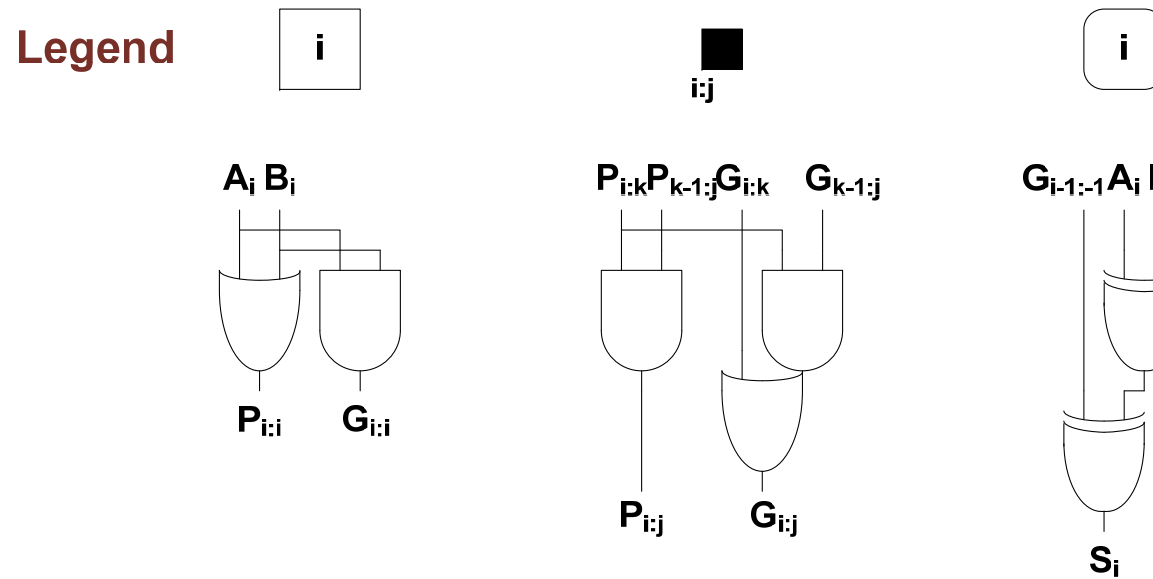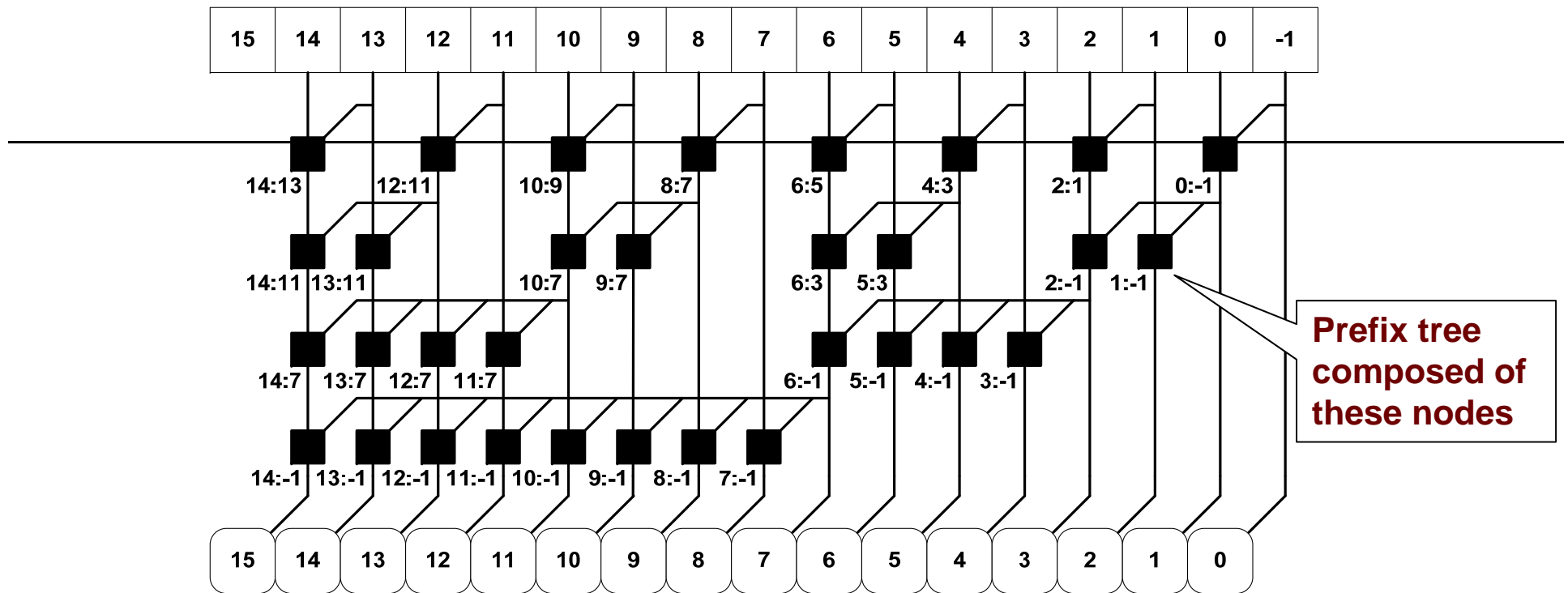
## ■ Operational Semantics Overview:

- Carry-in either generated in a column or propagated from a previous column
- Column -1 holds  $C_{in}$ , so  **$G_{-1} = C_{in}$  and  $P_{-1} = 0$**
- Carry-in to column i equals carry-out of column i-1:  **$C_{i-1} = G_{i-1:-1}$**
- $G_{i-1:-1}$  is the generate signal spanning columns i-1 to -1
- Sum equation:  $S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$
- Goal: Quickly compute  $G_{0:-1}$ ,  $G_{1:-1}$ ,  $G_{2:-1}$ ,  $G_{3:-1}$ ,  $G_{4:-1}$ ,  $G_{5:-1}$ , ...
  - **These are called prefixes**





# Prefix Adder /3

---

- **Operational Semantics Continued:**

- Generate and propagate signals for a block spanning bits  $i:j$ :

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$

$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- **Generate Stage: block  $i:j$  will generate a carry if**

- Upper part ( $i:k$ ) generates a carry, or
- Upper part propagates a carry generated in lower part ( $k-1:j$ )

- **Propagate Stage: block  $i:j$  will propagate a carry if**

- Both the upper and lower parts propagate the carry

- See Section 5.2.1 of the Harris textbook for details

# Prefix Adder /4

---

## ■ Prefix Adder Delay

- For N-bit prefix adder (PA):

$$t_{PA} = t_{pg} + \log_2 N \times (t_{pg\_prefix}) + t_{XOR}$$

- $t_{pg}$  is the delay to produce  $P_i G_i$  (OR and AND gate)
- $t_{pg\_prefix}$  is the delay of black prefix cell (AND-OR gate)

- The delay grows logarithmically instead of linearly
- **An N-bit PA is generally faster than a CLA for  $N \geq 32$**

# Adder Delay Comparisons

---

- **Let us compare the delay of 32-bit ripple-carry, carry-lookahead, and prefix adders**

- CLA has 4-bit blocks

- 2-input gate delay = 100 ps; full adder delay = 300 ps

- $t_{\text{ripple}} = N \times t_{\text{FA}} = 32(300 \text{ ps}) = \mathbf{9.6 \text{ ns}}$

- $t_{\text{CLA}} = t_{\text{pg}} + t_{\text{pg\_block}} + (N/k - 1) \times t_{\text{AND\_OR}} + k \times t_{\text{FA}}$   
 $= [100 + 600 + (7)200 + 4(300)] \text{ ps} = \mathbf{3.3 \text{ ns}}$


- $t_{\text{PA}} = t_{\text{pg}} + \log_2 N \times (t_{\text{pg\_prefix}}) + t_{\text{XOR}}$   
 $= [100 + \log_2 32(200) + 100] \text{ ps} = \mathbf{1.2 \text{ ns}}$

# Subtractor


## ■ Subtraction:

- Subtract A from B by first changing the sign of B using an inverter (i.e., complement B's bits and then add 1)
- Then add A and the inverted B

### Symbol

 

### Implementation

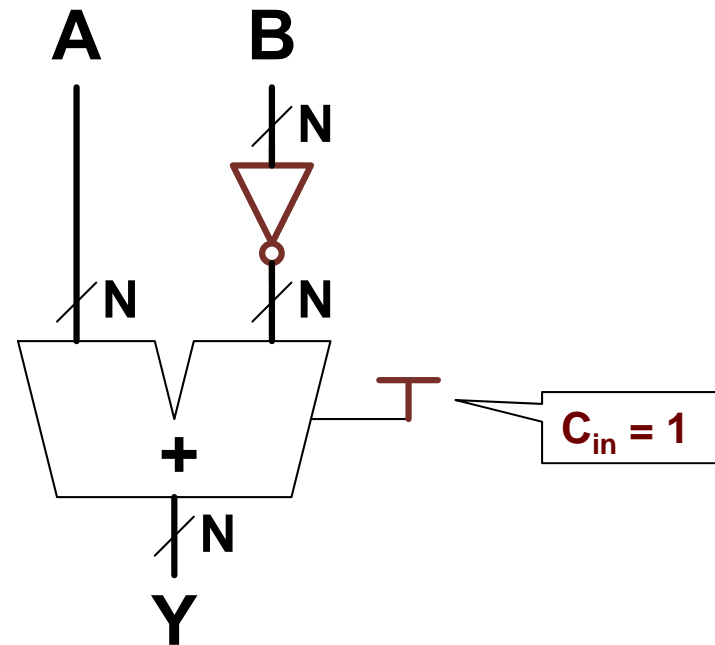

# Equality Comparator


## ■ Comparator:

- Determines if two N-bit binary numbers, A and B, are equal, or if one number is greater than or less than the other number


## ■ Equality Comparator:

- Produces a single output that indicates if A is equal to B

### Symbol

 


### Implementation

 
 
# Magnitude Comparator

- **Magnitude Comparator:**
  - Produces one or more outputs indicating the relative values of A and B
  - First compute  $A - B$  and then look at the MSB of the result
  - If the MSB equals 1 (i.e., the result is negative), A is less than B; otherwise, A is greater than or equal to B




# Introducing Arithmetic Logic Unit (ALU) /1

---

## ■ Arithmetic/Logical Unit (ALU):

- Combines mathematical and logical operations
- A typical ALU performs AND, OR, addition, subtraction, and magnitude comparison operations
- **The ALU is at the core of most computer systems**
- Certain ALUs produce extra outputs, called flags, that indicate information about the ALU output
- For example, overflow flag indicates that the result of the adder overflowed; zero flag indicates that the result is zero


## ■ The symbol for ALU:

 

where F is the selector bit that selects the corresponding operation



 
# Introducing Arithmetic Logic Unit (ALU) /2



$F_{2:0}$	Function
000	$A \& B$
001	$A   B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A   \sim B$
110	$A - B$
111	SLT

# Introducing Arithmetic Logic Unit (ALU) /3


$F_{2:0}$	Function
000	$A \& B$
001	$A   B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A   \sim B$
110	$A - B$
111	SLT

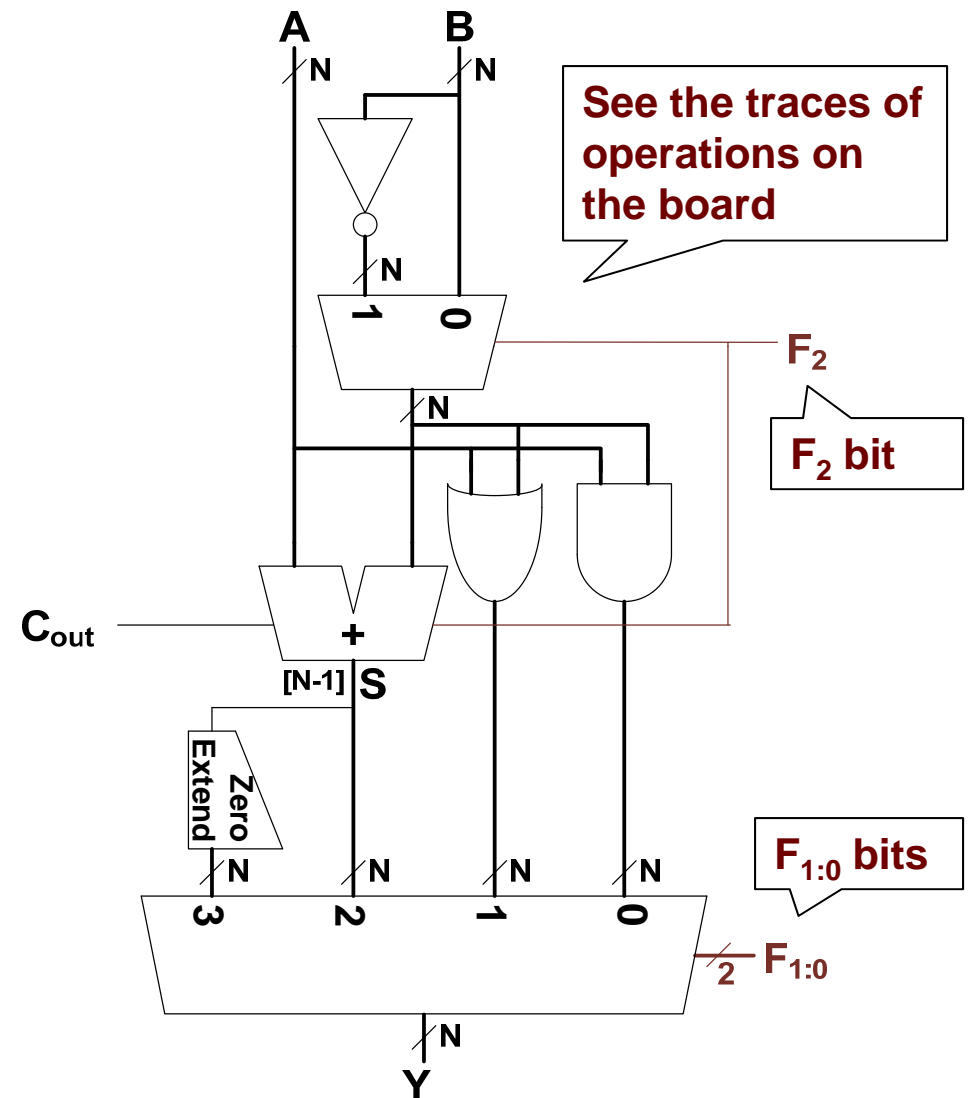

# Introducing Arithmetic Logic Unit (ALU) /4
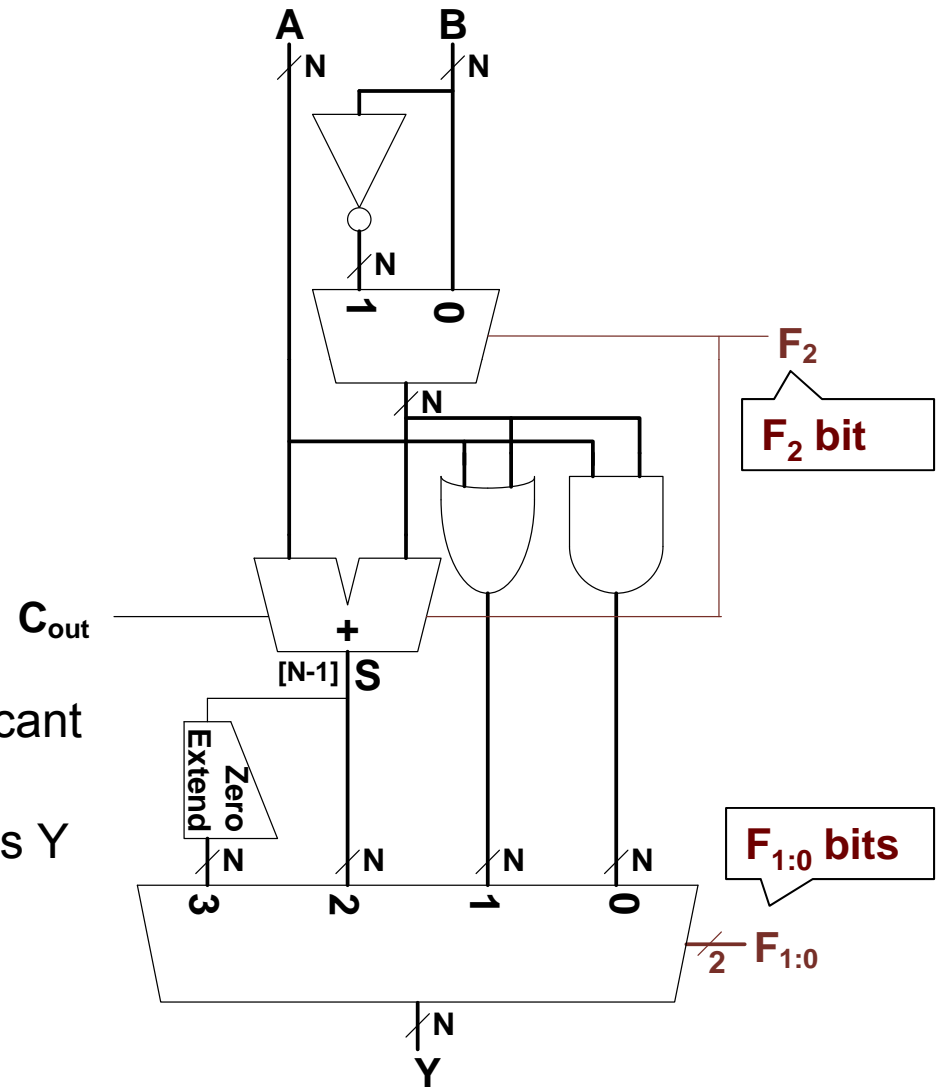
## ■ Configure 32-bit ALU for SLT operation:

- $A = 25$  and  $B = 32$
- $A < B$ , so  $Y$  should be 32-bit representation of 1 (0x00000001)
- $F_{2:0} = 111$ 
  - $F_2 = 1$  (adder acts as subtracter), so  $25 - 32 = -7$
  - $-7$  has 1 in the most significant bit ( $S_{31} = 1$ )
  - $F_{1:0} = 11$  multiplexer selects  $Y = S_{31}$  (zero extender) = 0x00000001



# Shifters and Rotators /1

---

## ■ Shifters and Rotators:

- Move bits and multiply or divide by powers of 2.
- **Shifter:** Circuit that shifts a binary number left or right by a specified number of bit positions
- **Rotator:** Rotates a binary number in a circle pattern, so that empty spots are filled with bits shifted from the other end
- **Logical Shifter:** Shifts a binary number to the left (`sll`) or right (`sr1`), and fills the empty bits with 0s
- **Arithmetic Shifter:** Performs the same as the logical shifter on left (`sll` and `sll` are the same); on right, it fill the bits with a copy of the MSB (`sra` is different than `sr1`)

# Shifters and Rotators /2

## ■ Shifters and Rotators Examples:

### ■ Logical shifter:

11001 >> 2 = 00110

11001 << 2 = 00100

### ■ Arithmetic shifter:


11001 >>> 2 = 11110

11001 <<< 2 = 00100

### ■ Rotator:



11001 ROR 2 = 01110

11001 ROL 2 = 00111

 
  
# Shifters and Rotators /3

- **shamt<sub>1:0</sub>:**
  - Represents the shift magnitude
  - The input, A, is shifted by shamt<sub>1:0</sub> bits, and routed to Y
  - If shamt<sub>1:0</sub> = 00, Y = A



# Shifters and Rotators /4

---

## ■ Shifters and Rotators Applied:

- $A \ll N = A \times 2^N$

$00001 \ll 2 = 00100 \quad (1 \times 2^2 = 4)$

$11101 \ll 2 = 10100 \quad (-3 \times 2^2 = -12)$

- $A \gg N = A / 2^N$

$01000 \gg 2 = 00010 \quad (8 / 2^2 = 2)$

$10000 \gg 2 = 11100 \quad (-16 / 2^2 = -4)$

- Trace these through the matching shifters on the next slide

# Multipliers /1

## ■ Multipliers:

- N-by-N multipliers multiply two N-bit numbers, and produce 2N-bit results
- **The partial products in binary multiplication are either the multiplicand or all 0s**
- Multiplication of 1-bit binary numbers is equivalent to the AND operation, so AND gates are used to form the partial products

### Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$


multiplicand  
multiplier  
partial  
products  
  
**result**

### Binary

$$\begin{array}{r} 0101 \\ \times 0111 \\ \hline 0101 \\ 0101 \\ 0101 \\ + 0000 \\ \hline 0100011 \end{array}$$

**Multiplying a single digit of the multiplier with multiplicand in stages**

 **Shifted partial products are then summed to form the result**



$$230 \times 42 = 9660$$

$$5 \times 7 = 35$$




$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 & A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \\
 & A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \\
 + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$

**Trace execution of  
0101 x 0101**

**Adders add components of  
the partial products**

 
**Shifting performed via  
the output bits**



# Divider Overview
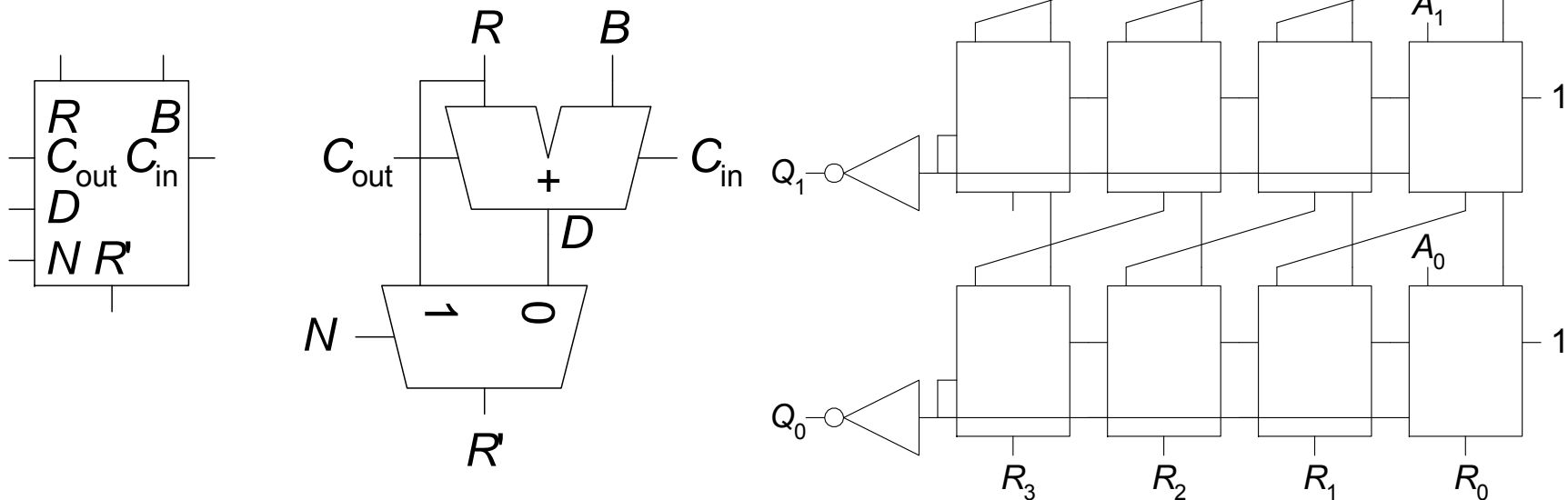
## ■ Divider Example:

- The divider computes  $A/B$  and produces a quotient,  $Q$ , and a remainder,  $R$
- $N$  indicates if  $R - B$  is negative, and it is obtained from the  $C_{out}$  bit of the left-most block



# Food for Thought

---

- **Download and Read Assignment #2 Specifications**
- **Read:**
  - Chapter 3 of the course textbook
    - Review the material discussed in the lecture notes in more detail
  - (Optional) Chapter 5 of the Harris and Harris textbook