

# Sequential Logic Design

---

Dr. Igor Ivkovic

iivkovic@uwaterloo.ca

[with material from “Computer Organization and Design” by Patterson and Hennessy, and “Digital Design and Computer Architecture” by Harris and Harris, both published by Morgan Kaufmann]

# Objectives

---

- Introduction to Sequential Logic Circuits
- Latches, Flip-Flops, and Registers
- Synchronous Logic Design
- Finite State Machines

# Sequential Logic Circuit /1

---

- **Sequential Logic Circuit – It Has Memory**

- Outputs of a sequential logic circuit depend on the current and the prior input values

- **State:**

- All the information about a circuit necessary to explain its future behavior

- **Latches and Flip-Flops:**

- State elements that store one bit of state

- **Synchronous Sequential Circuits:**

- Combinational logic followed by a bank of flip-flops

# Sequential Logic Circuit /2

---

## ■ Sequential Logic Circuits:

- Give sequence to events
- Have (short-term) memory
- Use feedback from output to input to store information

## ■ State Elements:

- The state of a circuit influences its future behavior
- State elements store the circuit state



## ■ State elements include:

- Bistable circuit
- SR Latch
- D Latch
- D Flip-flop

# Bistable Circuit /1
  
## ■ Bistable Circuit:

- Fundamental building block of other state elements
- Two outputs:  $Q$ ,  $\bar{Q}$
- No inputs



# Bistable Circuit /2


- **Consider the two possible cases:**

- $Q = 0$ : then  $\bar{Q} = 1$ ,  $Q = 0$  (stable)

- $Q = 1$ : then  $\bar{Q} = 0$ ,  $Q = 1$  (also stable); hence, called bistable

- Stores 1 bit of state in the state variable,  $Q$  (or  $\bar{Q}$ )

 - **But there are no inputs to control the state**




# SR (Set/Reset) Latch /1

---
 
## ■ SR (Set/Reset) Latch:

- Composed of two cross-coupled NOR gates
- It has two inputs, S and R, and two outputs, Q and  $\bar{Q}$




## ■ Consider the four possible cases:

- $S = 1, R = 0$
- $S = 0, R = 1$
- $S = 0, R = 0$
- $S = 1, R = 1$


# SR (Set/Reset) Latch /2
 
## ■ SR Latch analysis:

- $S = 1, R = 0$ :  
then  $Q = 1$  and  $\bar{Q} = 0$



 - $S = 0, R = 1$ :  
then  $\bar{Q} = 1$  and  $Q = 0$







# SR (Set/Reset) Latch /3

 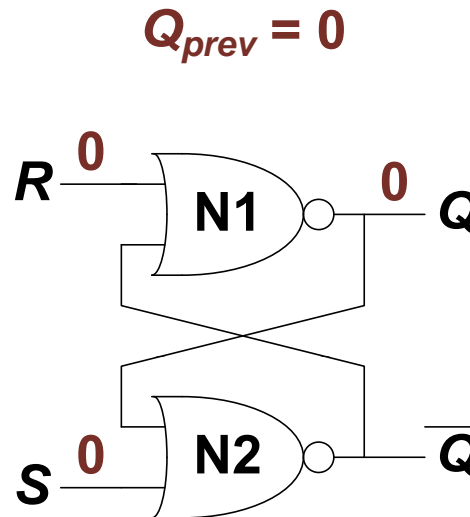
## ■ SR Latch

- $S = 0, R = 0$ :  
then  $Q = Q_{prev}$

- That is, we have **MEMORY** since  
 $Q = Q_{prev}$



 - $S = 1, R = 1$ :  
then  $Q = 0, \bar{Q} = 0$
- We have an **invalid state**  
since  $Q \neq \text{NOT } \bar{Q}$



# SR (Set/Reset) Latch /4


## ■ SR Latch Summary:

- Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S$ ,  $R$  as inputs
- Set: Make the output 1 ( $S = 1$ ,  $R = 0$ ,  $Q = 1$ )
- Reset: Make the output 0 ( $S = 0$ ,  $R = 1$ ,  $Q = 0$ )
- Must do something to avoid **invalid state** (when  $S = R = 1$ )

## ■ Can be implemented in different ways as long as it corresponds to the following truth table

$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q_{prev}$	$\bar{Q}_{prev}$
0	1	0	1
1	0	1	0
1	1	0	0

## SR Latch Symbol

 

# D Latch /1

---


## ■ D Latch:

- Sequential logic circuit element that separates the state data from the timing of state change
- Two inputs: clock input signal (CLK), data input signal (D)
- **CLK signal: controls when the output changes**
- **D signal/bit: controls to what the output changes**

## ■ Operational functionality:

- When CLK = 1, D passes through to Q (transparent)
- When CLK = 0, Q holds its previous value (opaque)
- **Avoids invalid case when  $Q \neq \overline{Q}$**

### D Latch Symbol

 



# D Latch /2

## ■ D Latch Internals:

Remembers the previous state if CLK = 0; otherwise Q equals D

<i>CLK</i>	<i>D</i>	$\overline{D}$	<i>S</i>	<i>R</i>	<i>Q</i>	$\overline{Q}$
0	X	$\overline{X}$	0	0	$Q_{prev}$	$\overline{Q_{prev}}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0

S and R cannot both be 1

  

# D Flip-Flop /1

---

## ■ D Flip-Flop:

- Sequential logic circuit built from two D latches controlled by CLK and its complement
- Two Inputs: CLK, D


## ■ Operational functionality:

- Samples D on the rising edge of CLK
- When CLK rises from 0 to 1, D passes through to Q
- Otherwise, Q holds its previous value
- Hence, Q changes only on the rising edge of CLK

## ■ Also called edge-triggered

- Since it is activated on the clock edge

## D Flip-Flop Symbols

 

# D Flip-Flop /2

## ■ D Flip-Flop explained:

- Two back-to-back latches (L1 and L2) controlled by the clock (CLK) signal and its complement

- **When CLK = 0**


- L1 is transparent
- L2 is opaque
- D passes through to N1

- **When CLK = 1**

- L2 is transparent
- L1 is opaque
- N1 passes through to Q

- Hence, on the edge of the clock (when CLK rises from 0 to 1)

- **D passes through to Q**


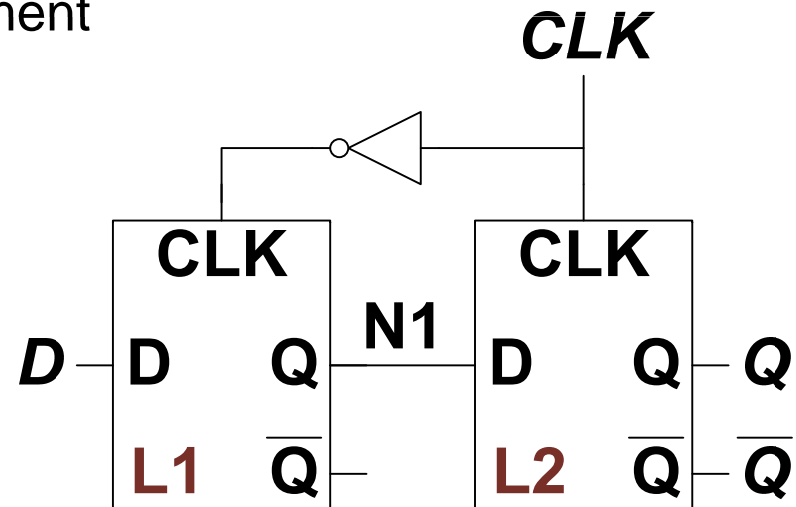


## ■ Fun Trivia:

- How many transistors are needed to build a typical D flip flop?
  - Hint: 2 transistors for NOT gate, 4 for NAND and NOR

# D Flip-Flop /3

## ■ D Latch vs. D Flip-Flop:

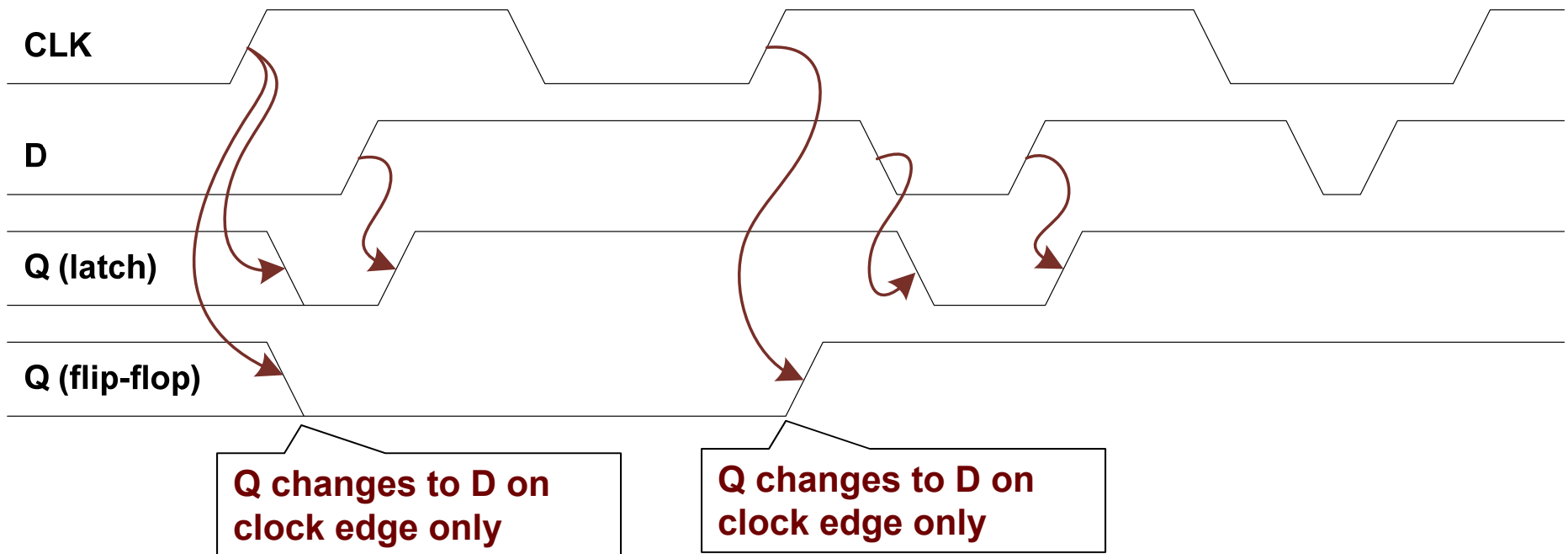 


# Register Introduced

- **N-bit Register:**

- A grouping of N flip-flops that share a common CLK input, so that all bits of the register are updated at the same time

- Example: 4-bit register

 



# Enabled Flip-Flop




## ■ Enabled D Flip-Flop:

- D passes through to Q only when enable (EN) is true
- Inputs: CLK, D, EN
- The enable input (EN) controls when new data (D) is stored

## ■ Operational functionality:

- EN = 1: D passes through to Q on the clock edge
- EN = 0: the flip-flop retains its previous state

### Symbol

   

# Set and Reset Flip-Flops



## ■ Set Flip-Flop:

- Inputs: CLK, D, Set

## ■ Operational functionality:

- Set = 1: Q is forced to 1
- Set = 0: flip-flop behaves as an ordinary D flip-flop

## Symbols

  



## ■ Reset Flip-Flop:

- Inputs: CLK, D, Reset

## ■ Operational functionality:



- Reset = 1: Q is forced to 0
- Reset = 0: flip-flop behaves as an ordinary D flip-flop

## Symbols

  
  
# Synchronous Logic Design /1

- Consider the following problematic circuit:



- No inputs and 1-3 outputs
- The circuit oscillates and it is not stable
- It has a cyclic path: output is fed back as input

# Synchronous Logic Design /2

---

- **Breaks cyclic paths by inserting registers**
  - Registers contain state of the system
  - State changes at clock edge: system synchronized to the clock
- **Rules of synchronous sequential circuit composition:**
  - Every circuit element is either a register or a combinational logic circuit
  - At least one circuit element is a register
  - All registers receive the same clock signal
  - Every cyclic path contains at least one register
- **Two common synchronous sequential circuits:**
  - Finite State Machines (FSMs)
  - Pipelines


# Synchronous Logic Design /3

## ■ Finite State Machine (FSM) consists of:

- State register
- Combinational logic

 
## ■ State register:

- Stores the current state
- Loads the next state at clock edge


 
## ■ Combinational (combinatorial) logic:


- Computes the next state
- Computes the outputs




# Finite State Machines /1

- **In a FSM:**
  - The next state is determined by the current state and inputs
- Two types of finite state machines differ in output logic:
  - **Moore FSM:** outputs depend only on the current state
  - **Mealy FSM:** outputs depend on the current state and inputs

## Moore FSM

 


## Mealy FSM

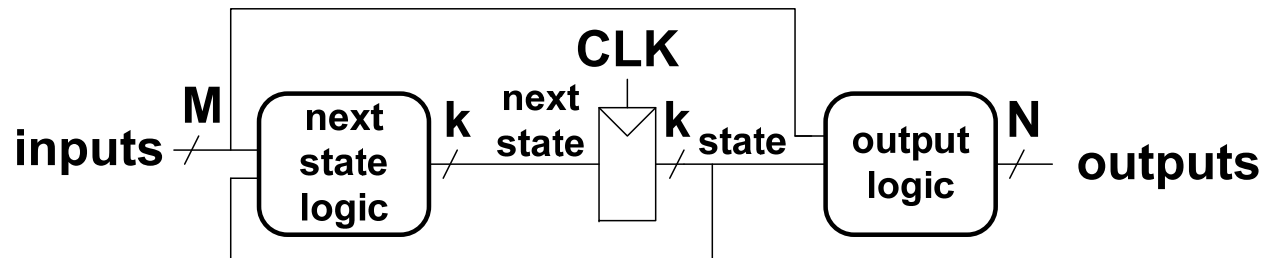

# Finite State Machines /2

---


## ■ Finite-State Digital Controller:

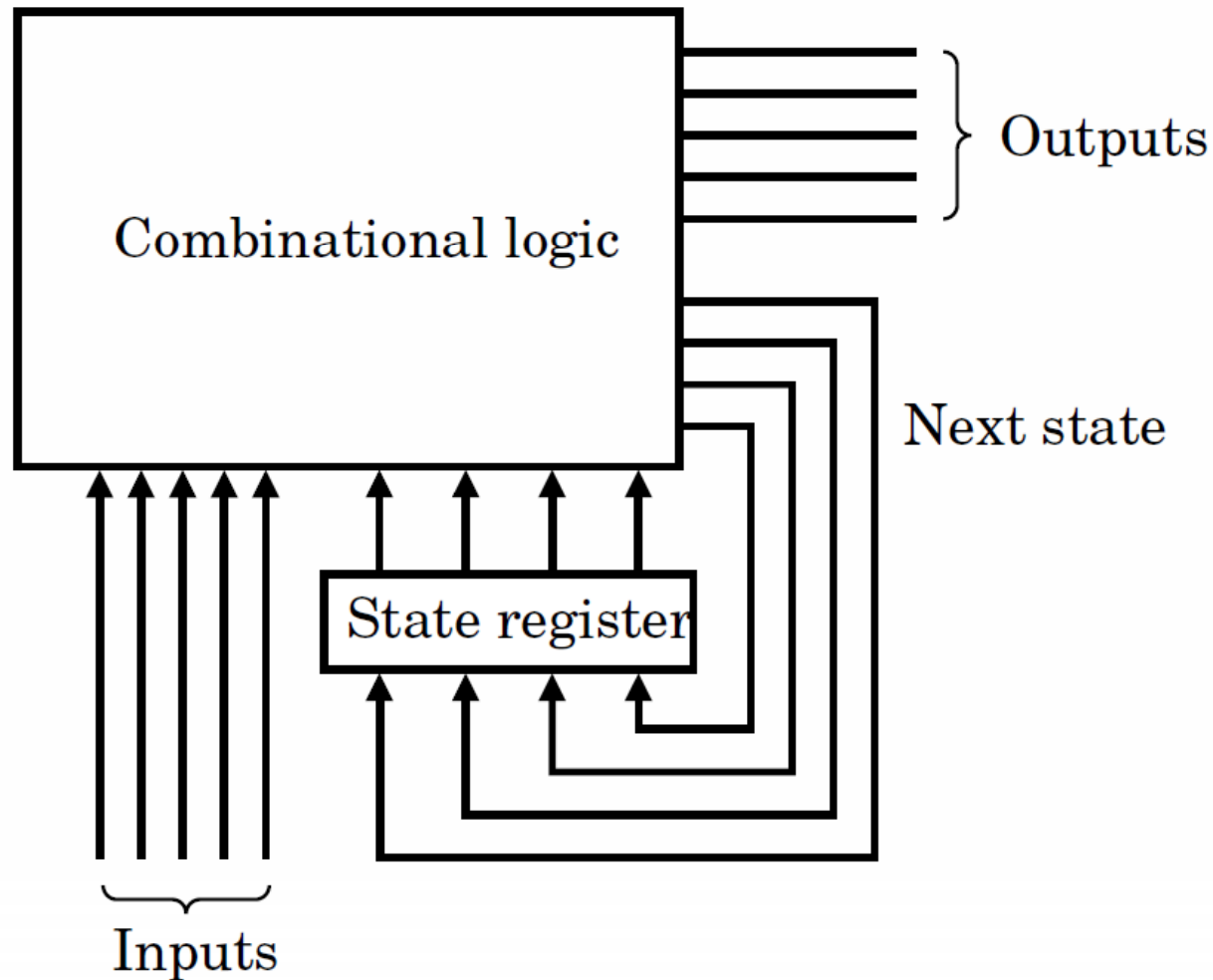

# Finite State Machines /3
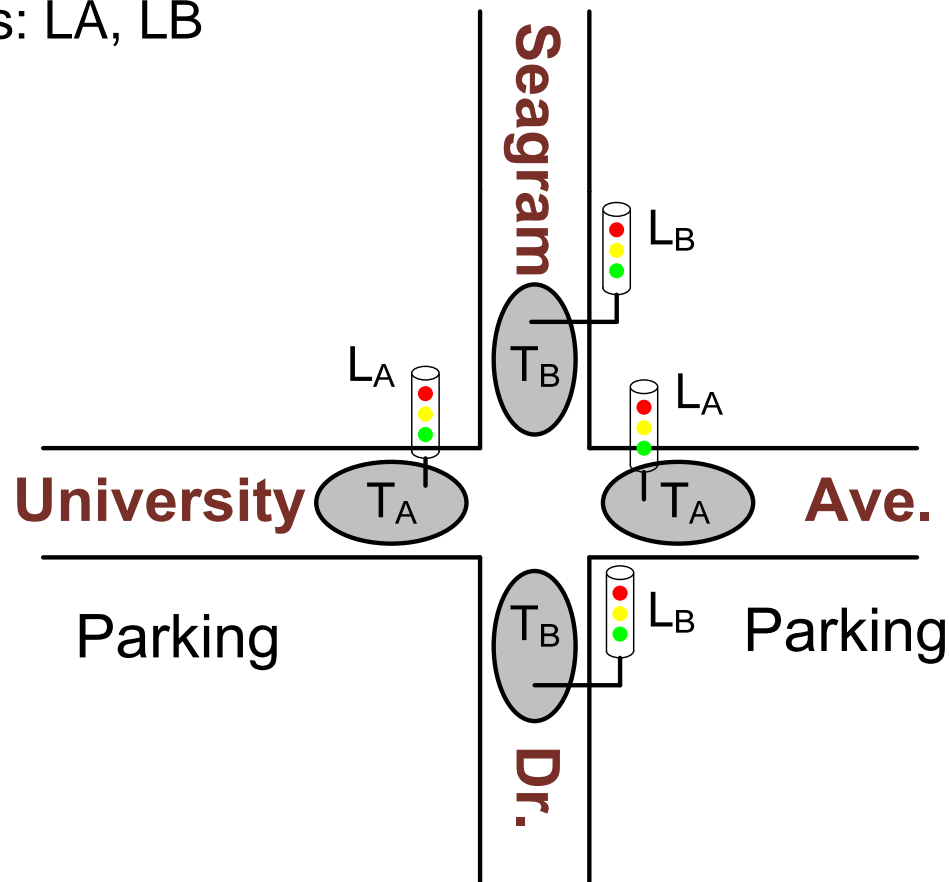
## ■ Traffic light problem:

- Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
- Lights:  $L_A$ ,  $L_B$







# Finite State Machines /4
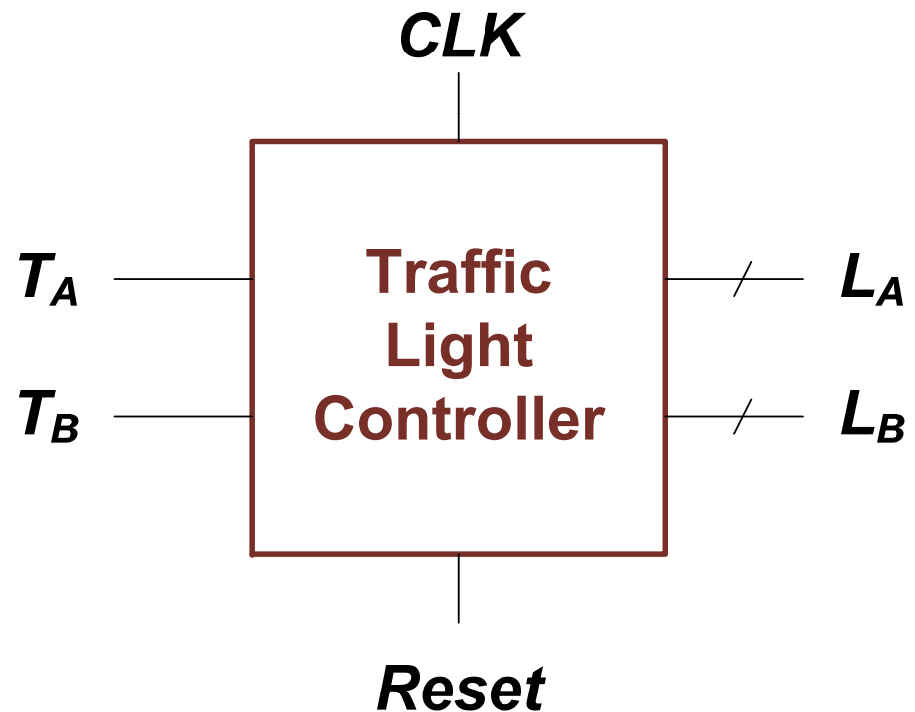 
## ■ Traffic light controller:



- Inputs: CLK, Reset,  $T_A$ ,  $T_B$
- Outputs:  $L_A$ ,  $L_B$



# Finite State Machines /5

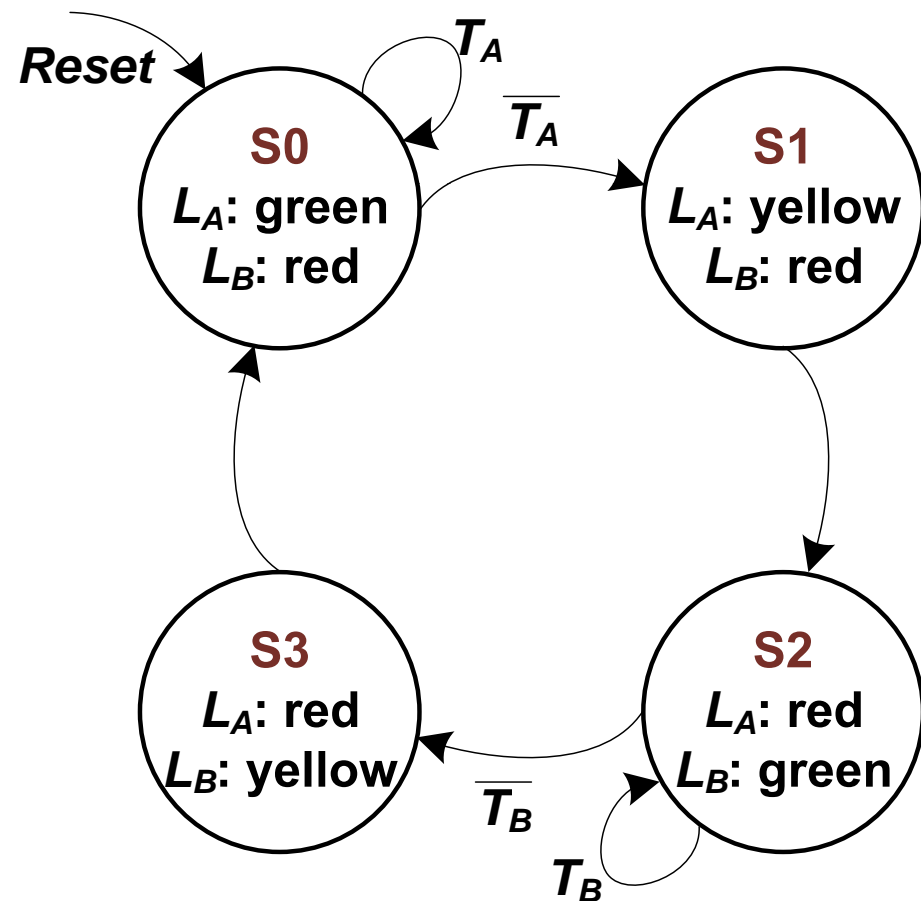 
## ■ Traffic light FSM:

- Moore FSM: outputs labeled in each state
- States: Circles
- Transitions: Arcs



# Finite State Machines /6

## ■ Traffic light FSM:

 

Current State $S$	Inputs		Next State $S'$
	$T_A$	$T_B$	
<b>S0</b>	<b>0</b>	<b>X</b>	<b>S1</b>
<b>S0</b>	<b>1</b>	<b>X</b>	<b>S0</b>
<b>S1</b>	<b>X</b>	<b>X</b>	<b>S2</b>
<b>S2</b>	<b>X</b>	<b>0</b>	<b>S3</b>
<b>S2</b>	<b>X</b>	<b>1</b>	<b>S2</b>
<b>S3</b>	<b>X</b>	<b>X</b>	<b>S0</b>

# Finite State Machines /7

## ■ FSM state encoding and state transition table:

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

# Finite State Machines /8

## ■ FSM output encoding and output table:

Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1}S_0$$

$$L_{B1} = \overline{S_1}$$


$$L_{B0} = S_1S_0$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

# Finite State Machines /9


---

## ■ FSM Schematic: State Register

 

# Finite State Machines /10

## ■ FSM Schematic: Next State Logic

 


$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} T_A + S_1 \overline{S_0} T_B$$

# Finite State Machines /11

## ■ FSM Schematic: Output Logic

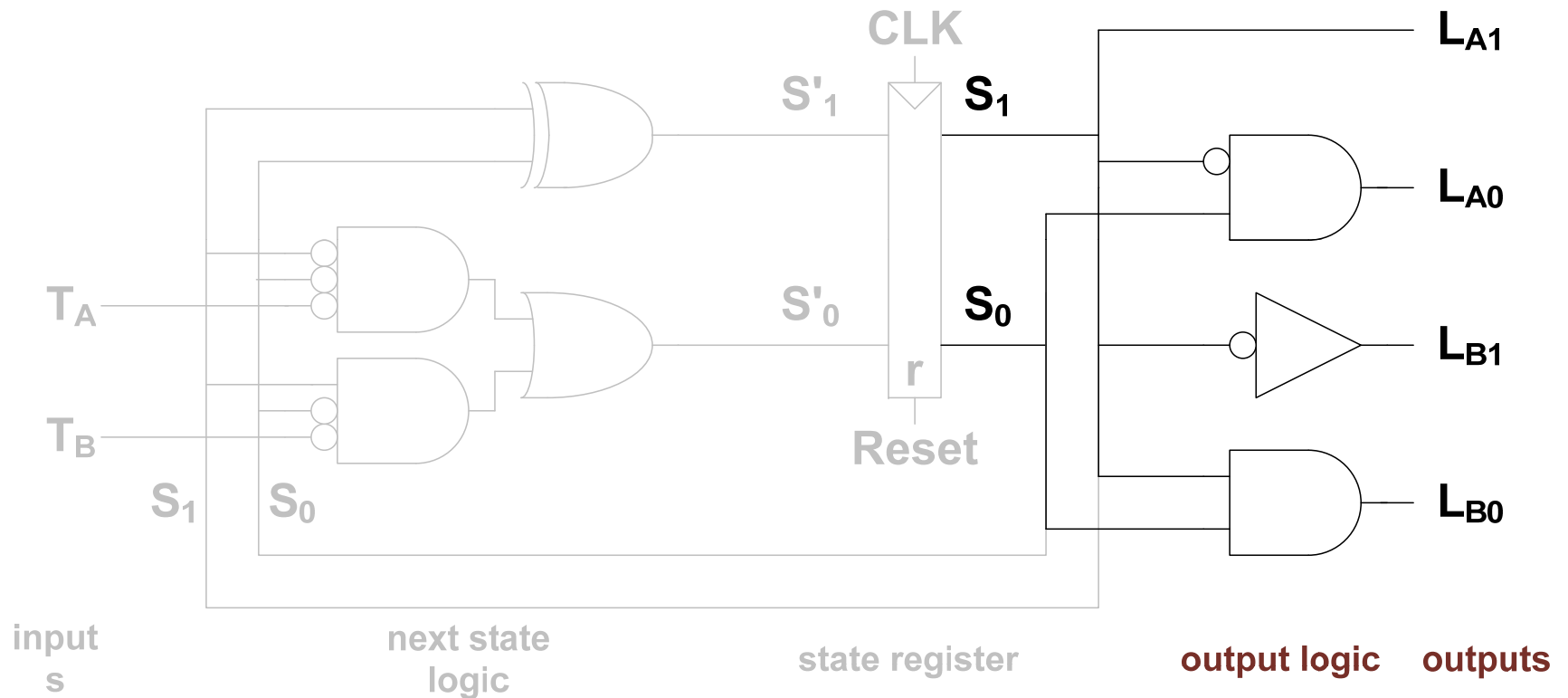

$$\begin{aligned}
 L_{A1} &= S_1 & L_{B1} &= \overline{S_1} \\
 L_{A0} &= \overline{S_1} S_0 & L_{B0} &= S_1 S_0
 \end{aligned}$$



# Finite State Machines /12

---

- **FSM binary state encoding:**

- For four states: 00, 01, 10, 11

- **FSM one-hot encoding:**


- One state bit per state
- Only one state bit is true at one time
- For four states: 0001, 0010, 0100, 1000
- One-hot encoding can run at higher clock rate but it requires more circuitry (i.e., a flip-flop for each bit)

# More on Finite State Machines /1

---
 
## ■ **Snail's Brain Example:**

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it
- The snail smiles whenever the last two digits it has crawled over are 01
- Design Moore FSM of the snail's brain




# More on Finite State Machines /2

## ■ Snail's Brain Example:

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it
- The snail smiles whenever the last two digits it has crawled over are 01
- Design Moore and Mealy FSMs of the snail's brain


## Moore FSM

 

# More on Finite State Machines /3

## ■ Snail's Brain Example:

### Moore FSM

 

State	Encoding
S0	00
S1	01
S2	10

Current State		Inputs A	Next State	
$S_1$	$S_0$		$S'_1$	$S'_0$
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0

$$S'_1 = S_0 A$$


$$S'_0 = \overline{A} (\overline{S_1} + \overline{S_0}) = \overline{A}$$

Not always true;  
but why here?

# More on Finite State Machines /4

## ■ Snail's Brain Example:

### Moore FSM

 

Current State		Output
$S_1$	$S_0$	$Y$
0	0	0
0	1	0
1	0	1


$$Y = S_1$$

# More on Finite State Machines /5

## ■ Snail's Brain Example:

- Mealy FSM: arcs indicate input/output

### Mealy FSM

 

State	Encoding
S0	00
S1	01


Current State	Input	Next State	Output
$S_0$	$A$	$S'_0$	$Y$
0	0	1	0
0	1	0	0
1	0	1	0
1	1	0	1

$$Y = S_0 A$$

$$S'_0 = \overline{A}$$


# More on Finite State Machines /6

## ■ Moore FSM Schematic:

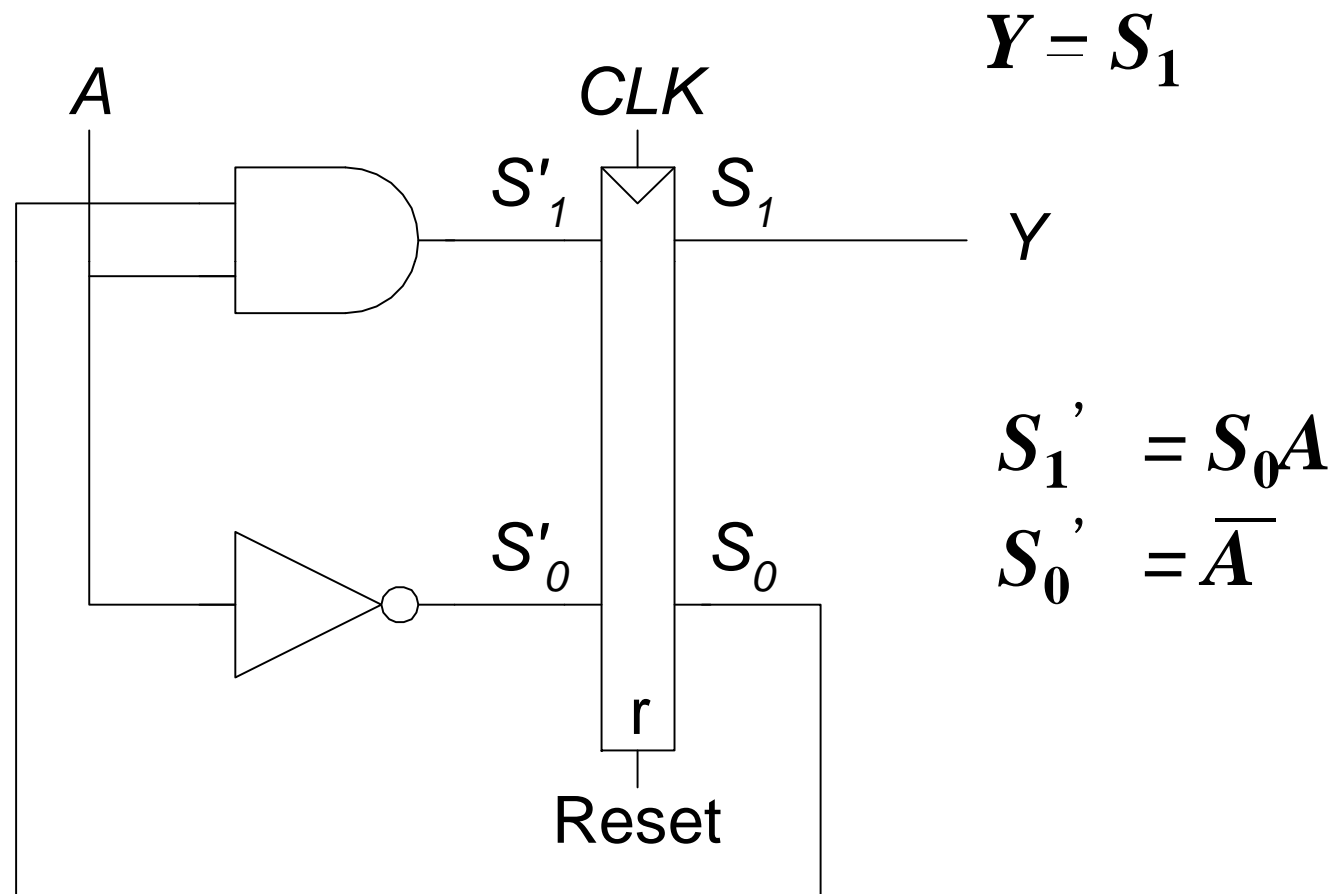

# More on Finite State Machines /7

## ■ Mealy FSM Schematic:

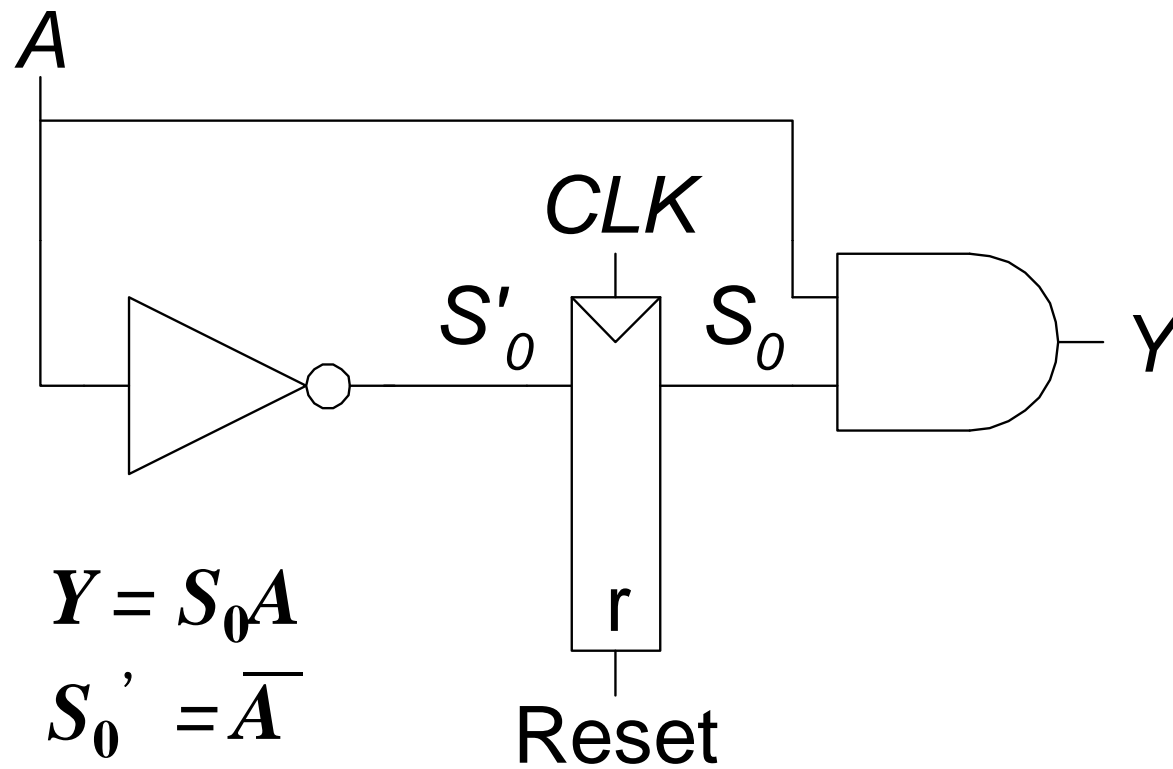



# More on Finite State Machines /8

---

## ■ **Designing FSMs Summary:**

1. Identify inputs and outputs
2. Sketch a state transition diagram
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Sketch the circuit schematic

# Factoring State Machines /1

---

- **Factoring a FSM:**

- Break a complex FSMs into smaller interacting FSMs

- **Example:**


- Modify traffic light controller to add Special Mode
- Two more inputs: P, R
- When  $P = 1$ , enter the Special Mode and Seagram Dr. light stays green (e.g., under construction, special University events)
- When  $R = 1$ , leave the Special Mode

# Factoring State Machines /2

## ■ Unfactored FSM:




## ■ Factored FSM:

 


# Factoring State Machines /3

## ■ Unfactored FSM:

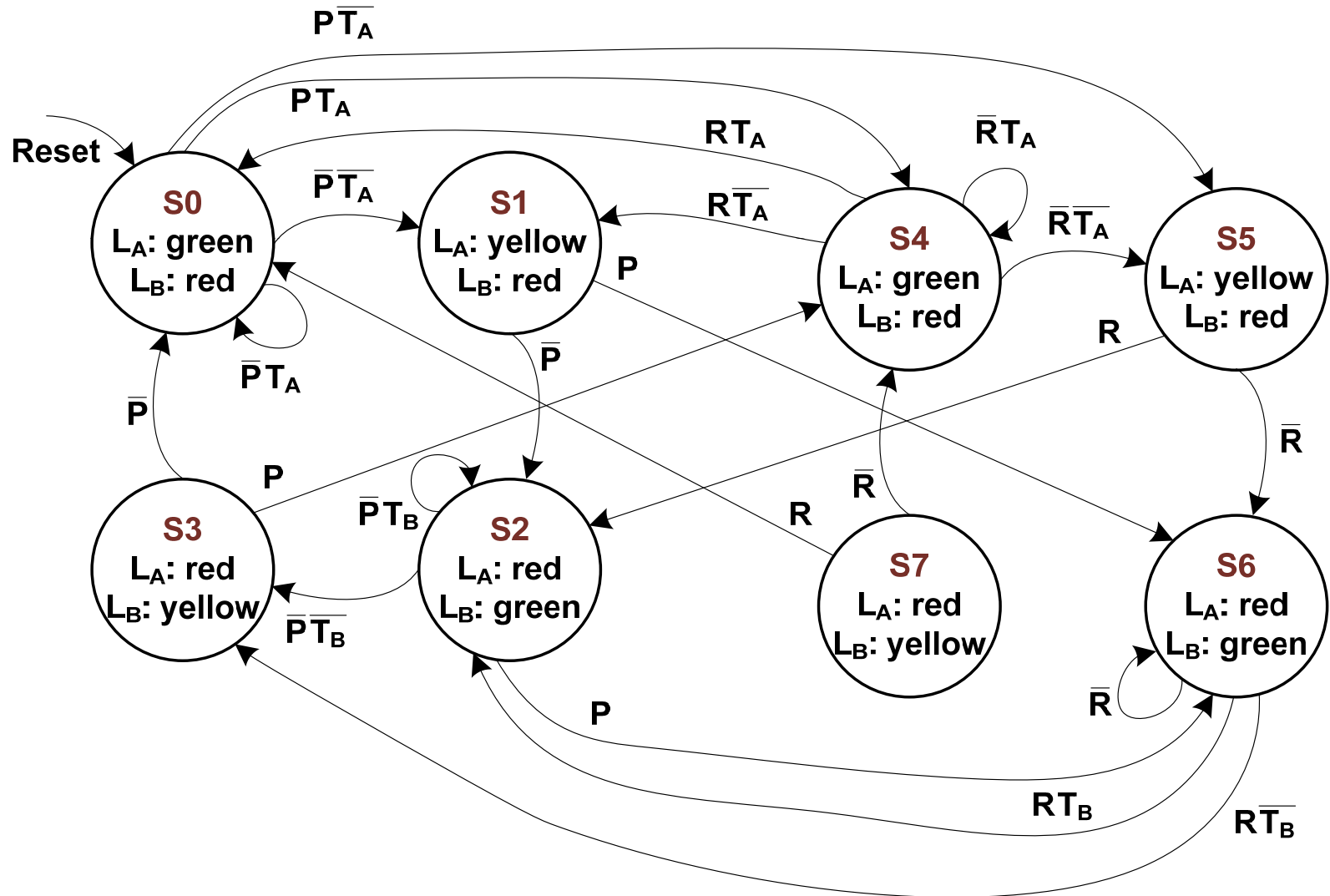


# Factoring State Machines /4

## ■ Factored FSM:

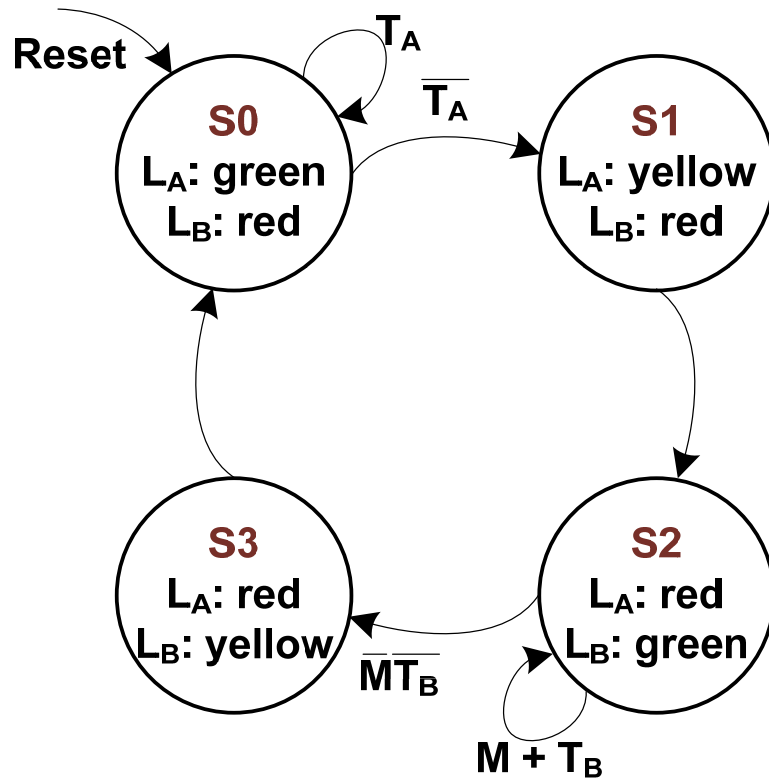

Lights FSM

 

Mode FSM

# Food for Thought

---

## ■ **Download and Read Assignment #1 Specifications:**

- Assignment #1 is intended as an introduction to the combinatorial logic design

## ■ **Read:**

- Appendix C and Appendix D of the course textbook
  - Review the material discussed in the lecture notes in more detail
- (Optional) Chapter 3 of the Harris and Harris textbook